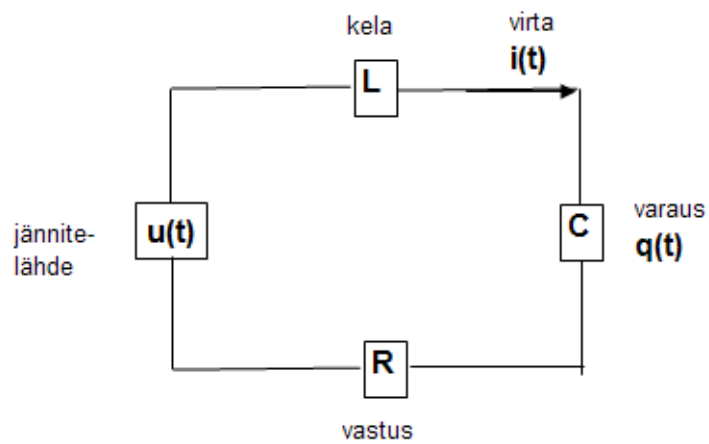



1. (*RLC*-circuit) Use SIMULINK to draw the graphs




of the voltages

$$U_C = q(t)/C, U_R = Ri(t), \text{ ja } U_L = Li'(t)$$

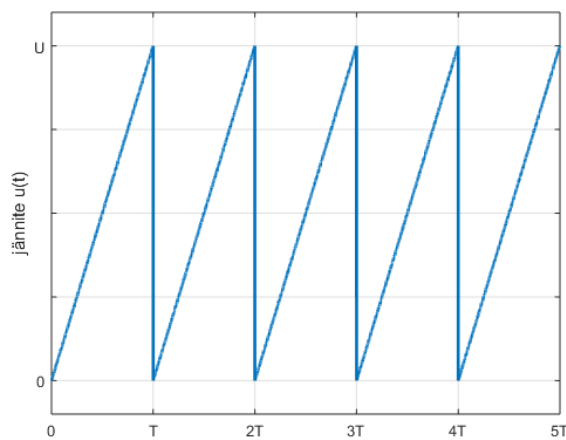on the interval $t = 0 \dots 5T$, when $u(t)$ is the saw tooth below (and for example, $L = 2, R = 1, C = 0.1, U = 10$ ja $T = 5$)



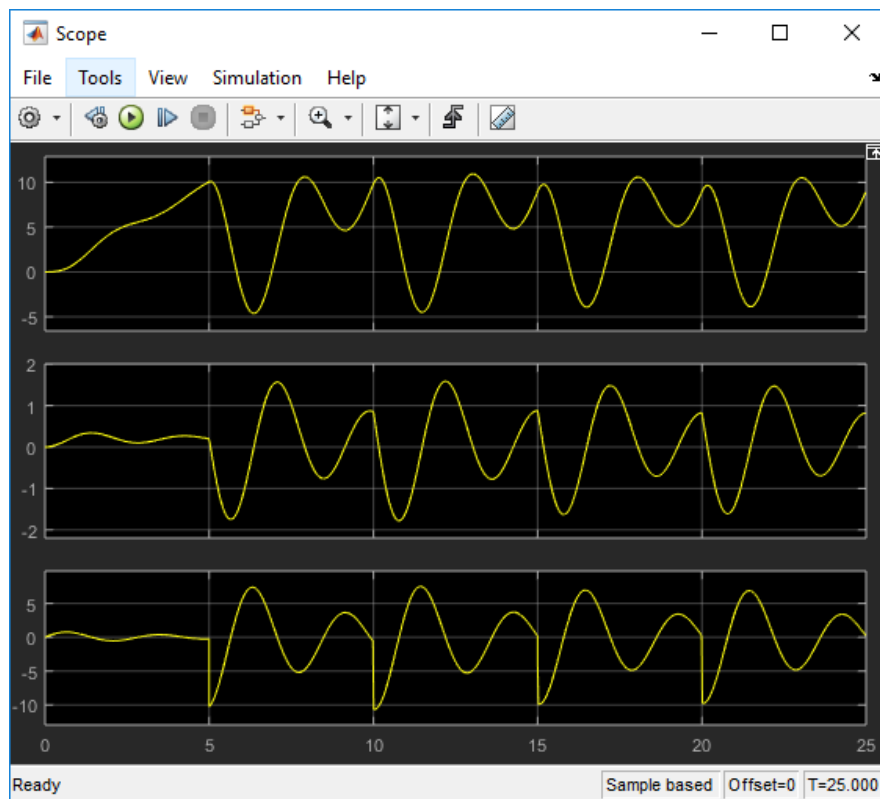

ohje: differential equation



$$L \cdot q''(t) + R \cdot q'(t) + \frac{1}{C} \cdot q(t) = u(t), \quad q(0) = 0, \quad q'(0) = 0$$

multiplication by a number: block Gain from math operations

differentiation: block Derivative from continuous

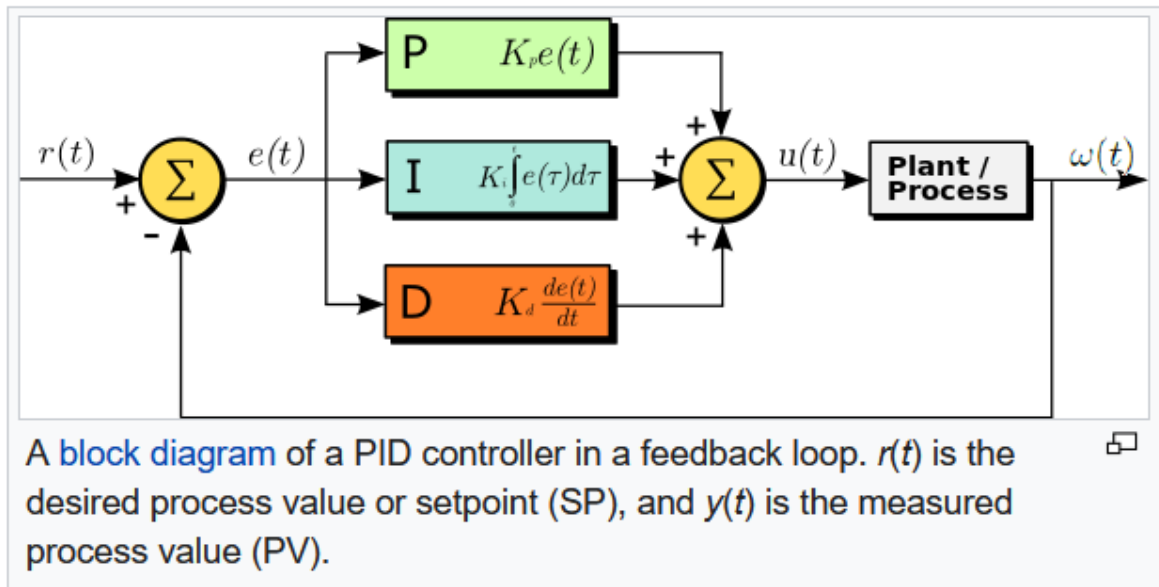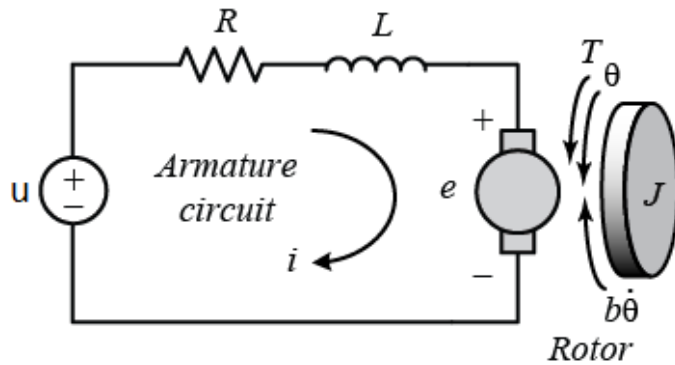2. (DC-motor) Use SIMULINK to draw the graphs of $e(t)$, $u(t)$ and $\omega(t)$, when $r(t) = 1$ and the differential equation is

$$JL\omega''(t) + (RJ + bL)\omega'(t) + (bR + K^2)\omega(t) = Ku(t)$$



$$J = 0.1, L = 0.5, R = 0.3, b = 0.08, K = 0.1$$

$$K_p = 5, K_i = 2, K_d = 0.001$$

