


1. ( $RL$ -circuit) Given  $R, L$  and  $U$ , solve the current  $i(t)$  from the equation


$$L \cdot i'(t) + R \cdot i(t) = u(t)$$

when  $u(t) = U$  and  $i(0) = 0$ , and draw the graphs of the voltages

$$U_R = R \cdot i(t) \text{ and } U_L = L \cdot i'(t)$$

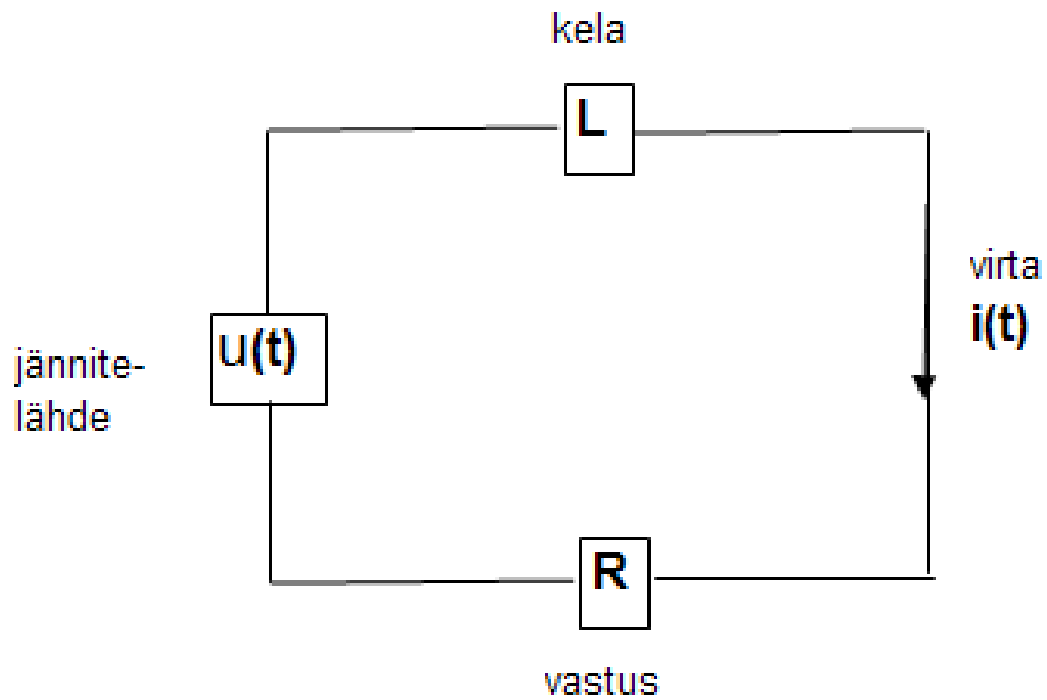on the interval  $t = 0 \dots 5\tau$ , where time constant  $\tau = L/R$ .




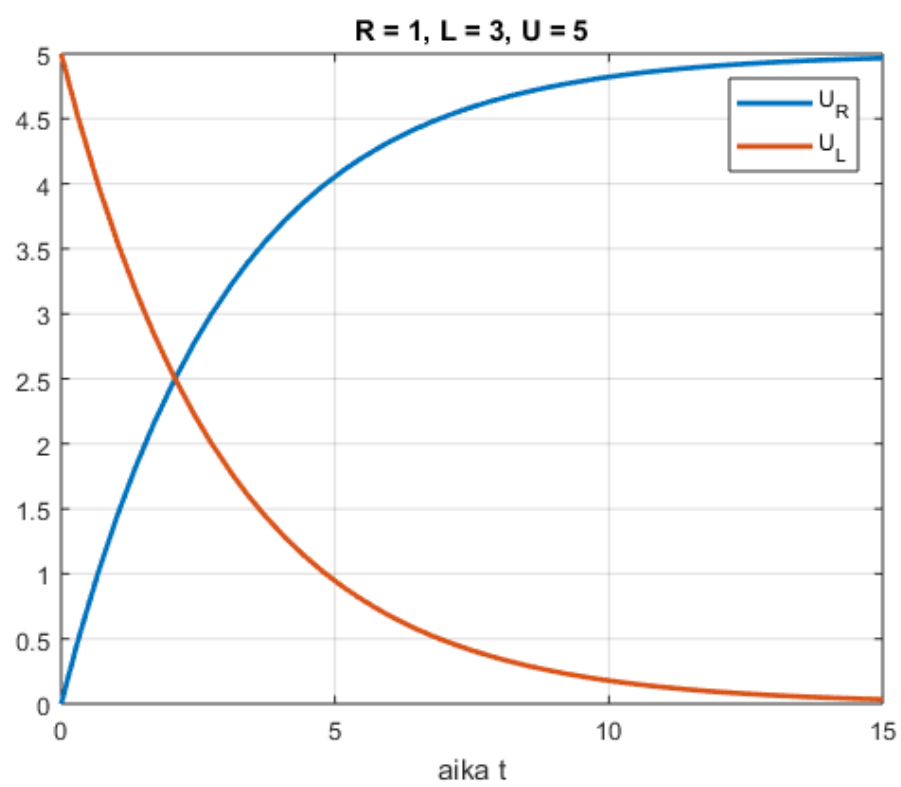

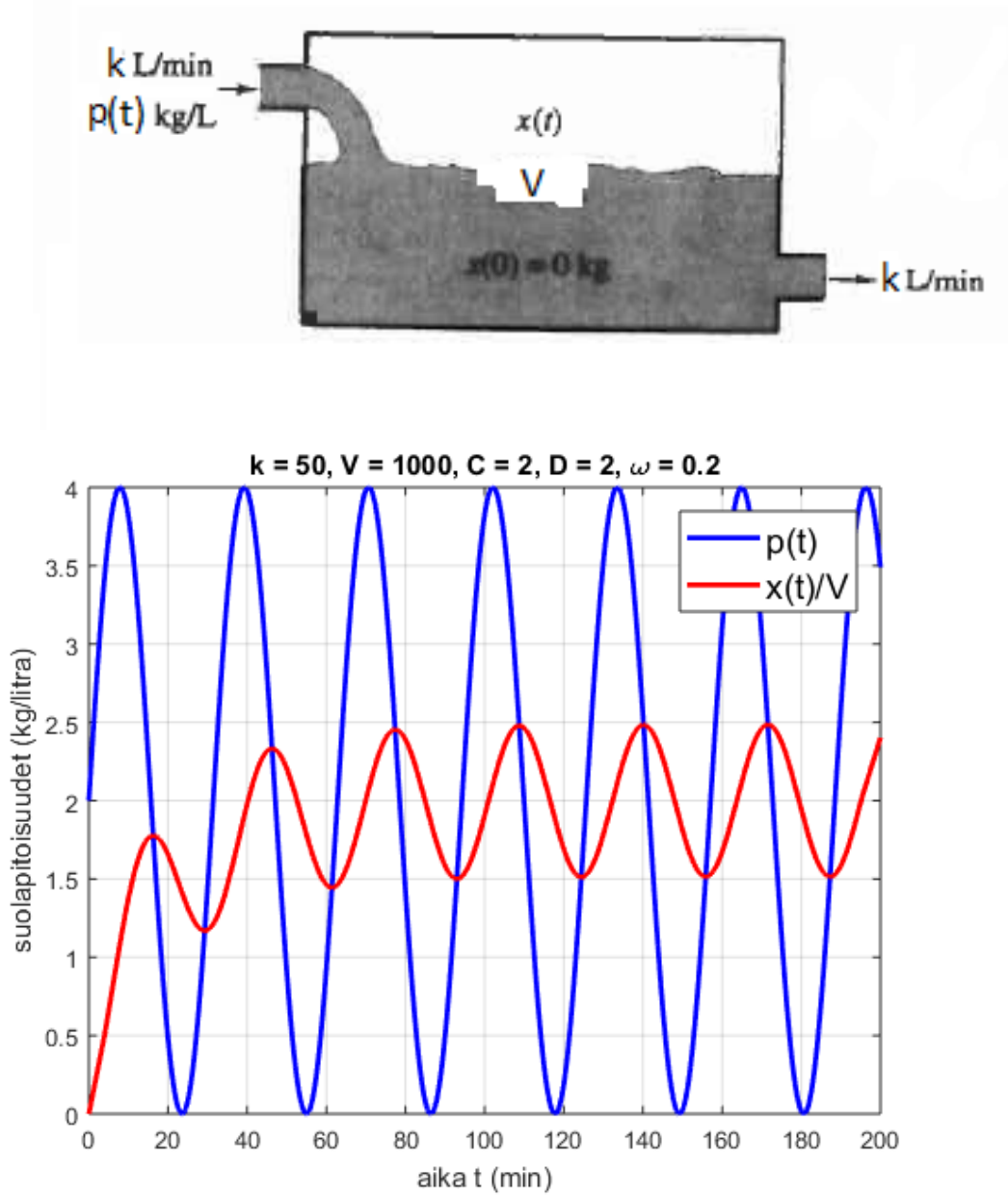2. Given the volume  $V$  (liters) of the tank, flow rate  $k$  (liters/min), amplitude  $C$ , constant  $D$  and angular frequency  $\omega$  of the incoming salt content (kg/liter)

$$p(t) = C \sin(\omega t) + D$$


solve the mass  $x(t)$  (kg) of the salt in the tank and draw the graphs of salt contents  $x(t)/V$  and  $p(t)$  on the interval  $t = 0 \dots 10/\tau$ , where  $\tau = k/V$



Deduce from the solution formulas that the salt content

$$\frac{x(t)}{V} \approx K \cdot C \sin(\omega t + \theta) + D, \text{ as } t \text{ increases}$$

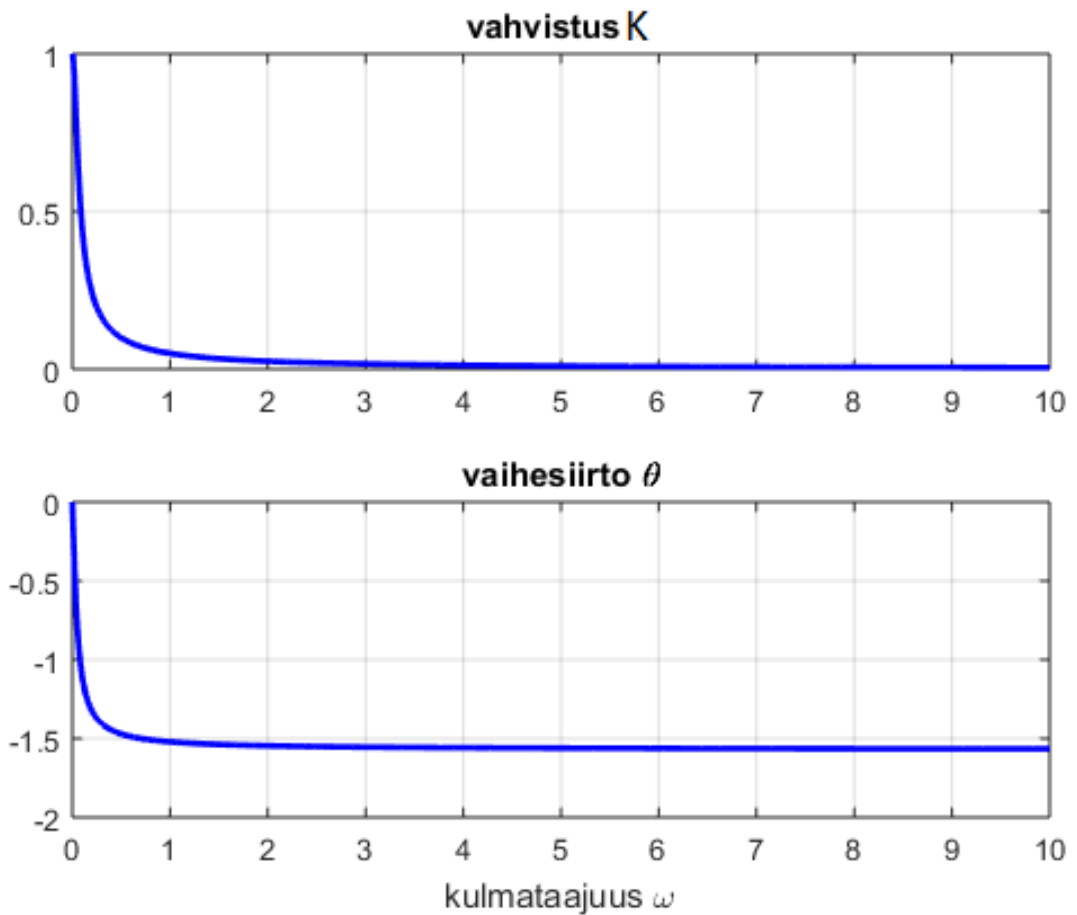and draw the graphs of the amplification  $K$  and phase shift  $\theta$  on the interval  $\omega = 0 \dots 100$




**3.** (*RLC*-circuit) Given  $R, L, C, U$  and  $T$ , solve  $q(t)$  from the equation



$$L \cdot q''(t) + R \cdot q'(t) + \frac{1}{C} \cdot q(t) = U, \quad q(0) = 0, \quad q'(0) = 0$$

and draw the graphs of the voltages


$$U_R = R i(t), \quad U_L = L i'(t) \quad \text{and} \quad U_C = q(t)/C$$

on the interval  $t = 0 \dots T$ .

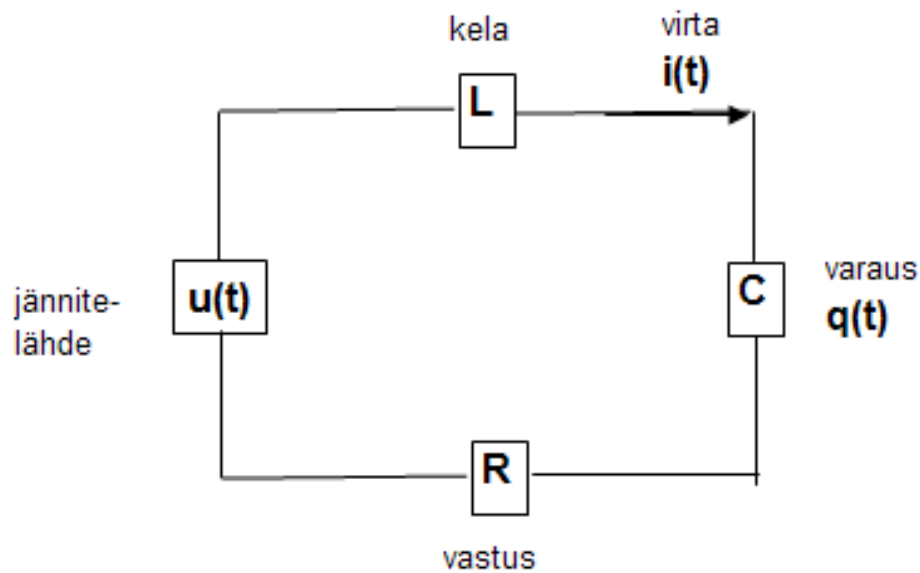

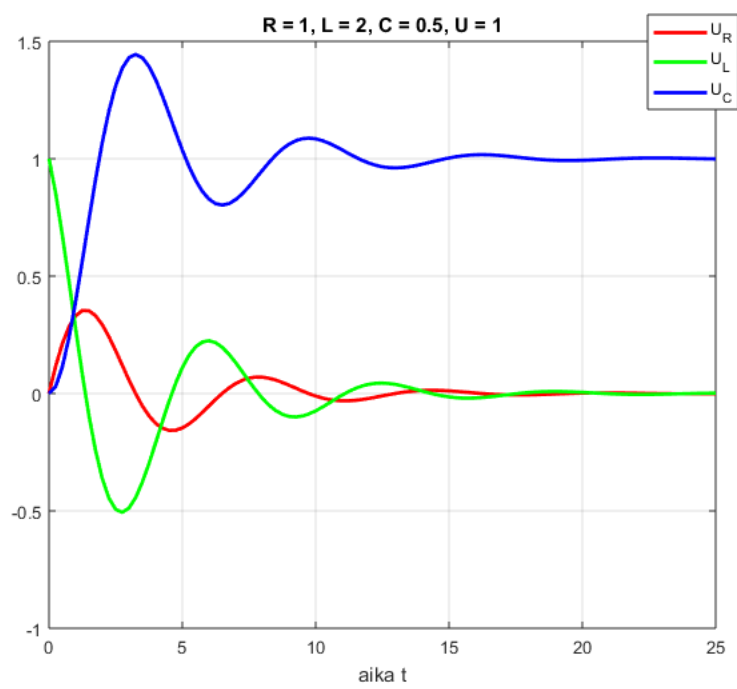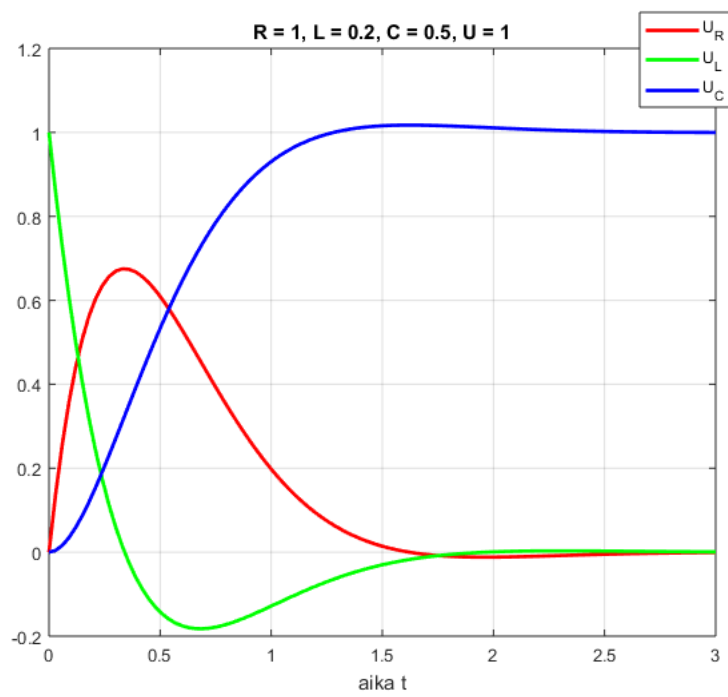


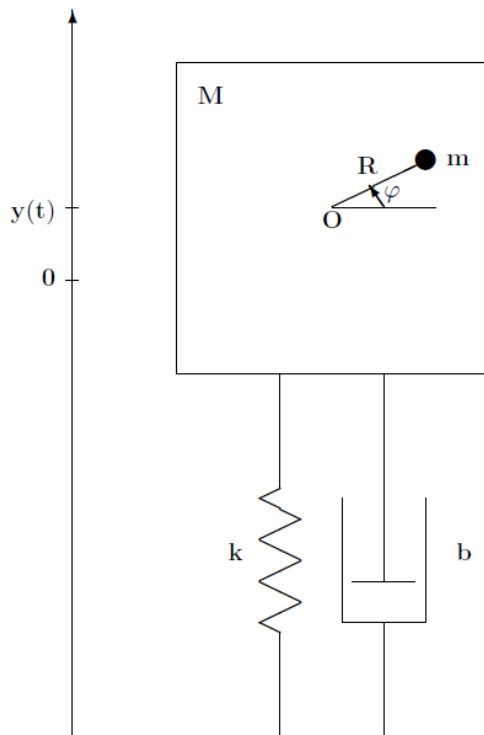
4. Mass  $m$  is rotating at angular speed  $\omega$  (rad/sec),  $M$  is the total mass,  $y(t)$  is the height of the center point  $O$



Given  $M, m, k, b, R$  and  $\omega$ , solve  $y(t)$  from the equation

$$M y''(t) + b y'(t) + k y(t) = m R \omega^2 \sin(\omega t), \quad y(0) = 0, \quad y'(0) = 0$$

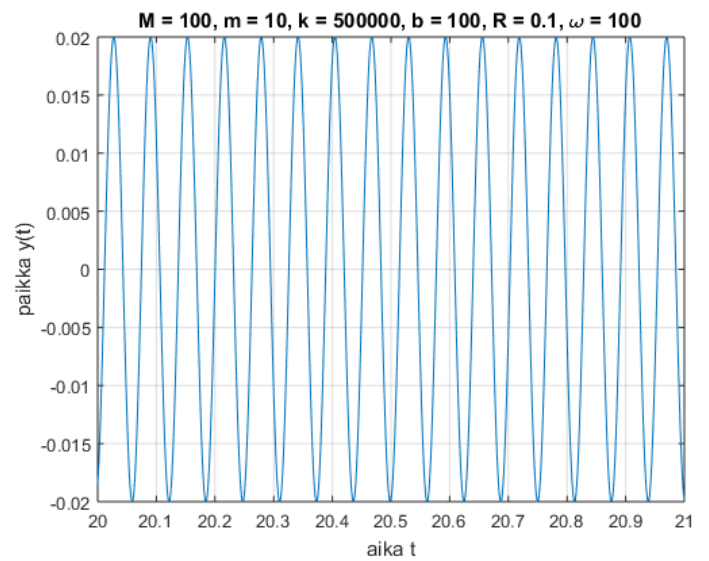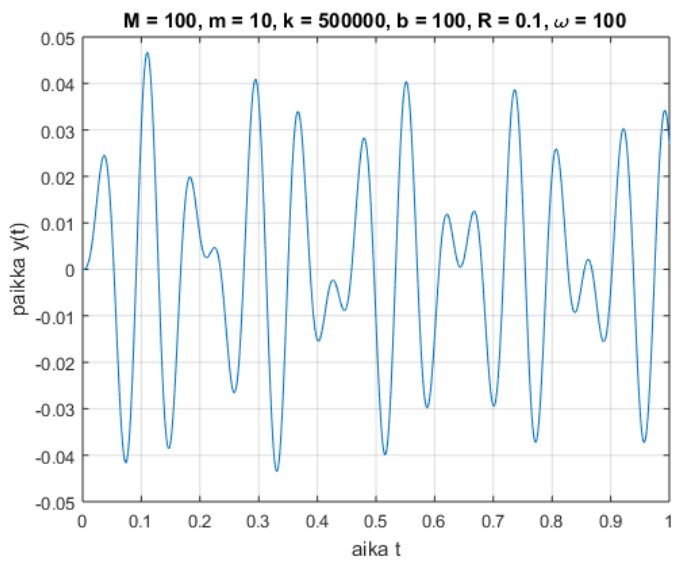
and draw its graph (on a suitable interval of  $t$ ).



Deduce from the solution formulas, that



$$y(t) \approx KA \sin(\omega t + \theta), \text{ as } t \text{ increases}$$

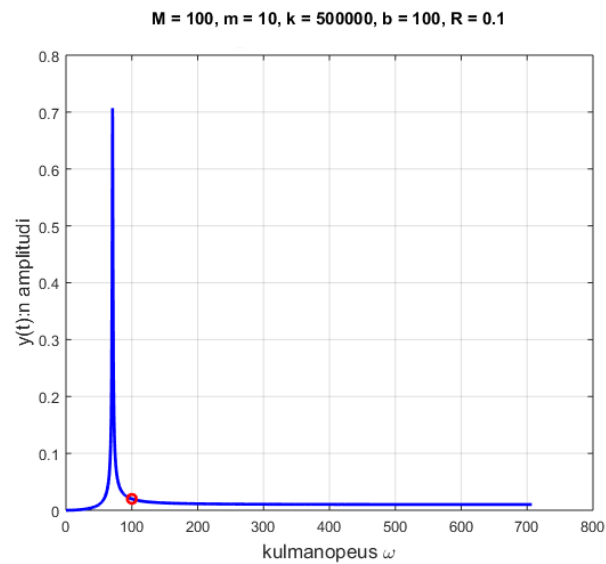and draw the graph of the amplitude  $KA$  on the interval  $\omega = 0 \dots 10\sqrt{k/M}$





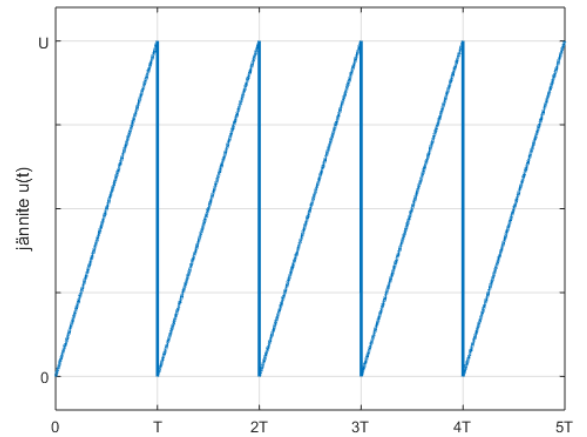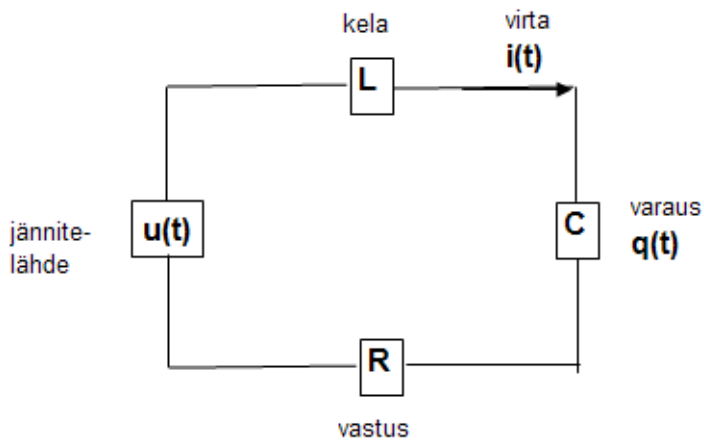5.  $RLC$ -circuit, input voltage  $u(t)$  the saw tooth below





Given  $R, L, C, U$  and  $T$ , calculate the values of  $q(t)$ ,  $i(t) = q'(t)$  and  $i'(t) = q''(t)$  numerically using the equation

$$L \cdot q''(t) + R \cdot q'(t) + \frac{1}{C} \cdot q(t) = u(t), \quad q(0) = 0, \quad q'(0) = 0$$

and draw the graphs of the voltages



$$U_R = R i(t), \quad U_L = L i'(t) \quad \text{ja} \quad U_C = q(t)/C$$

on the interval  $t = 0 \dots 5T$

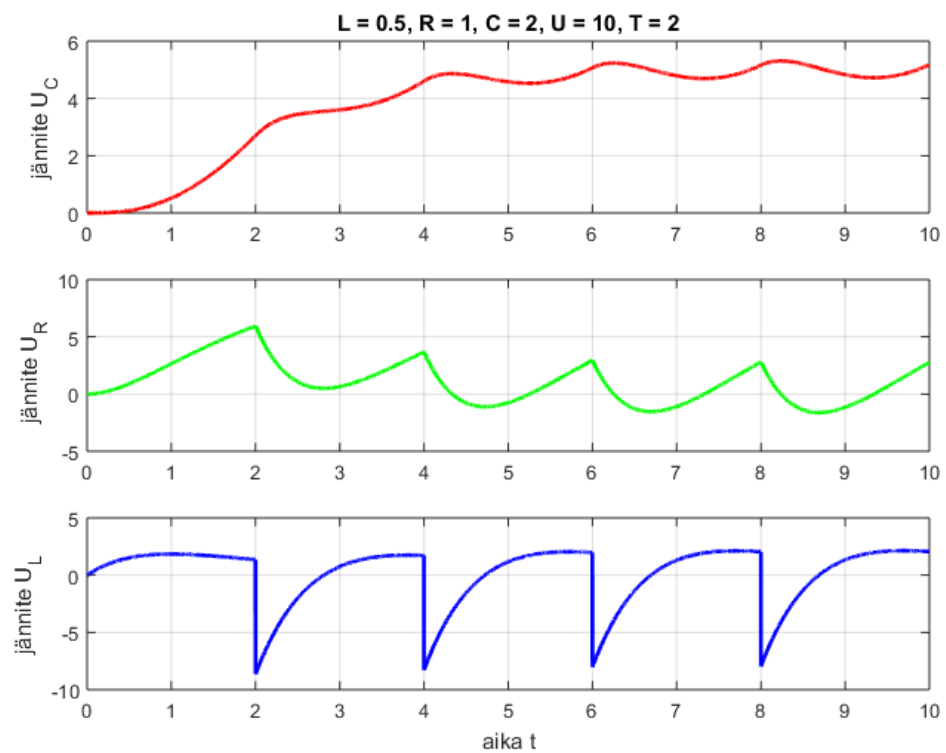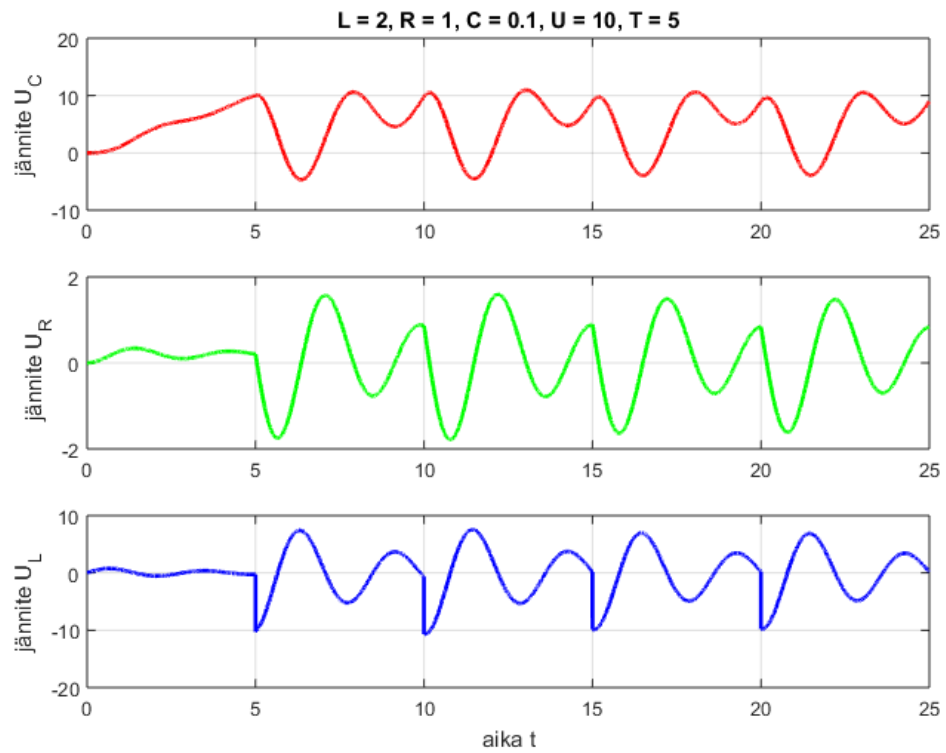

hint: ex 8

## 6. DC-motor

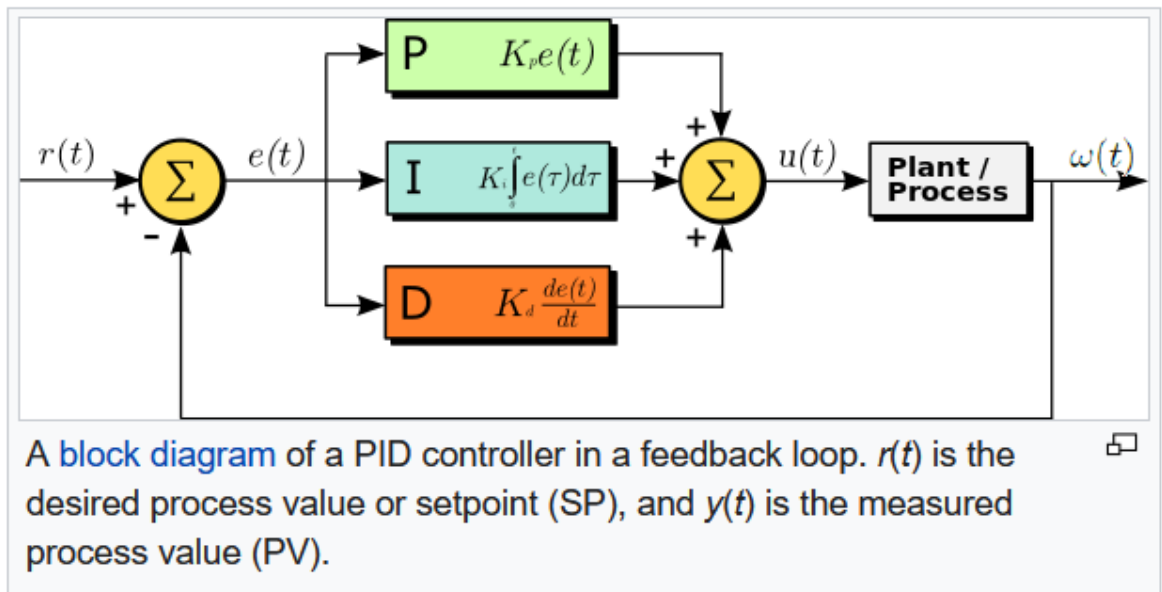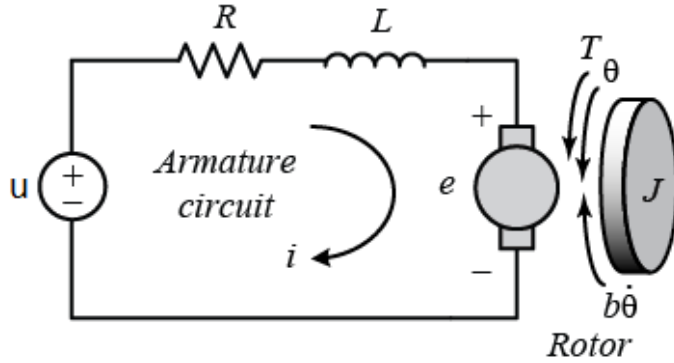

Given  $J, L, R, b, K, K_p, K_i, K_d$ , calculate the values of the PID-controlled angular speed  $\omega(t)$  using the equation

$$JL\omega''(t) + (RJ + bL)\omega'(t) + (bR + K^2)\omega(t) = Ku(t)$$

$$\omega(0) = 0, \omega'(0) = 0$$

when setpoint  $r(t) = 1$ , and draw the graphs of  $\omega(t)$ , error  $e(t) = r(t) - \omega(t)$  and the output  $u(t)$  of the PID-controller

$$J = 0.1, L = 0.5, R = 0.3, b = 0.08, K = 0.1$$

$$K_p = 5, K_i = 2, K_d = 0.001$$

